

IS 151 TEST 1 (Jan 2016)

1. Mention three equivalent ways of representing a Boolean function/expression **(3 Marks)**
2. What are 3 common useful functions that can be performed by digital logic circuits? **(3 marks)**
3. Simplify the following Boolean expressions using Karnaugh maps
 - (a) $A'B'C'D' + A'B'CD' + AB'C'D' + AB'CD'$ **(1 mark)**
 - (b) $ABC + BCD' + A'BC$ **(1 mark)**
4. Using Boolean algebra rules simplify the following expressions:
 - (a) $(A'BC')' + (AB'C)'$
 - (b) $C(B + C)(A + B + C)$
 - (c) $A'B + AB' + AB$
 - (d) $A'BC + AB'C + ABC' + ABC$**(4 Marks)**
5. Convert the following binary numbers to decimal:
 - (a) 110101
 - (b) 1110101**(2 Marks)**
6. Convert the following decimal numbers to binary:
 - (a) 368
 - (b) 125**(2 Marks)**
7. Convert the following hexadecimal numbers to binary
 - (a) 3AF
 - (b) 12C9**(2 Marks)**
8. Construct a truth table for each of the following Boolean expressions:
 - (a) $ABC' + A'B'C' + A'BC' + AB'C$ **(1 Mark)**
 - (b) $AB + AC + BC$ **(1 Mark)**
9. A combinational circuit has 3 inputs A, B, C and output F. F is true for the following input combinations:
 - A is False, B is True
 - A is False, C is True
 - A, B, C are False
 - A, B, C are True
 - (a) Write the Truth table for F. Use the convention True=1 and False=0 **(1 Mark)**
 - (b) Write the simplified expression for F in SOP form **(1 Mark)**
 - (c) Write the simplified expression for F in POS form **(1 Mark)**
 - (d) Draw the logic circuit diagram of F **(1 Mark)**
10. Construct the truth table and draw the logic circuit diagram of a Half Adder (HA) **(6 Marks)**